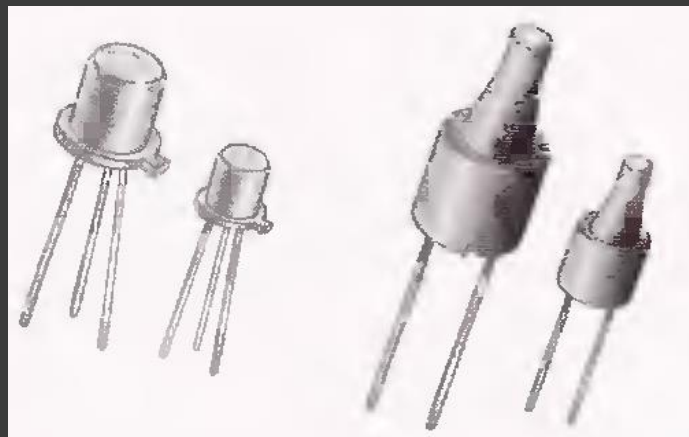


*Topic:*  
**PHOTOTRANSISTOR**

**By**  
**Dr. Vivek Ambalkar**



## INTRODUCTION


- ⦿ *The phototransistor is a transistor in which base current is produced when light strikes the photosensitive semiconductor base region.*
- ⦿ *The collector-base P-N junction is exposed to incident light through a lens opening in the transistor package.*
- ⦿ *When there is no incident light, there is only a small thermally generated collector-to-emitter leakage current i.e.  $I_{(CEO)}$ , this is called the dark current and is typically in the nA range.*

- When light strikes the collector-base pn junction, a base current is produced that is directly proportional to the light intensity.
- Since the actual photo generation of base current occurs in the collector-base region, the larger the physical area of this region, the more base current is generated.
- A phototransistor does not activated at every type of wave lengths of light.

- ❑ The phototransistor is similar to a regular BJT except that the base current is produced and controlled by light instead of a voltage source.
- ❑ The phototransistor effectively converts variations in light energy to an electrical signal
- ❑ The collector-base pn junction is exposed to incident light through a lens opening in the transistor package.
- ❑ The phototransistor is a transistor in which base current is produced when light strikes the photosensitive semiconductor base region.
- ❑ When there is no incident light, there is only a small thermally generated collector-to-emitter leakage current i.e.  $I_{CEO}$ , this is called the dark current and is typically in the range of nA.


- ❑ When light strikes the collector-base pn junction, a base current,  $I_{\lambda}$ , is produced that is directly proportional to the light intensity.
- ❑ This action produces a collector current that increases with  $I_{\lambda}$ .
- ❑ Except for the way base current is generated, the phototransistor behaves as a conventional BJT.
- ❑ In many cases there is no electrical connection to the base
- ❑ The relationship between the collector current and the light-generated base current in a phototransistor is  $I_C = \beta_{DC} * I_{\lambda}$ .


*SYMBOL OF*  
*PHOTOTRANSISTOR*

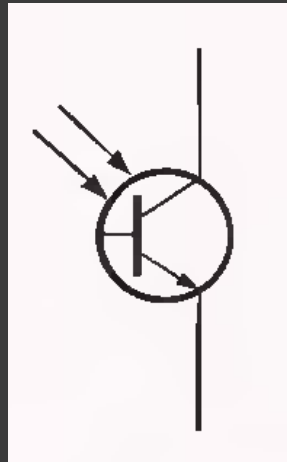

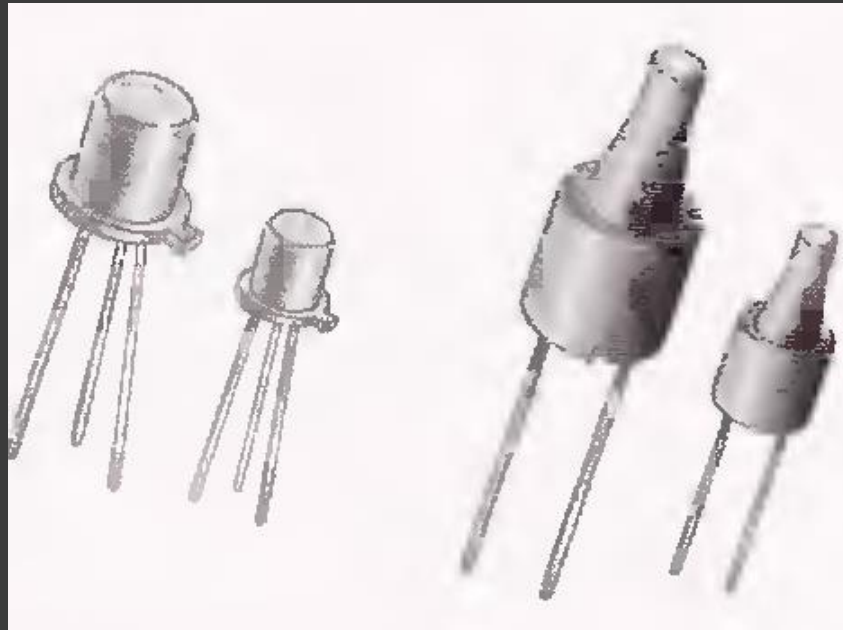**Schematic symbol**

*A typical phototransistor is designed to offer a large area to the incident light, as the simplified structure diagram in Figure:*



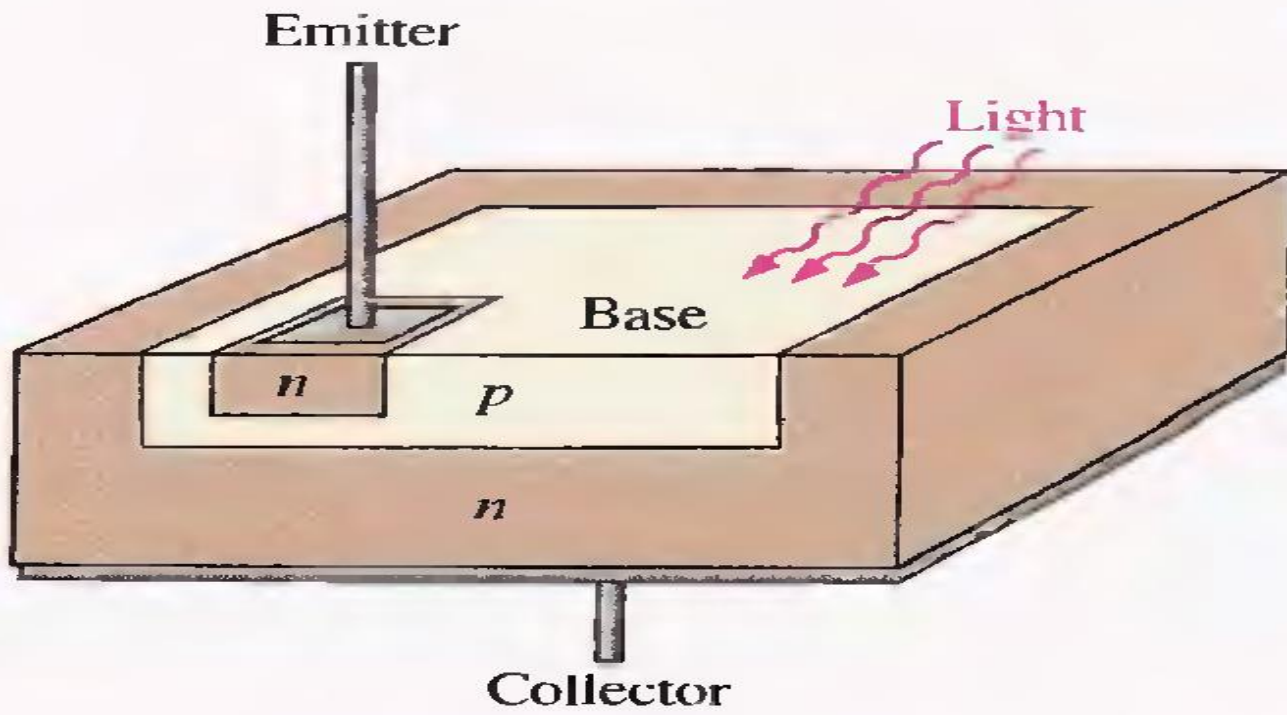




Phototransistor are of two types.

1. Three Lead Phototransistor.
2. Two Lead Phototransistor.

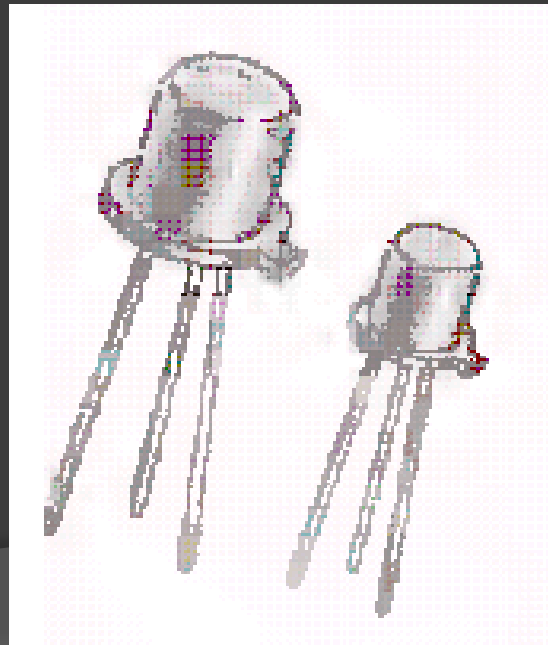
# 1. Three Lead Phototransistor:


*In the three-lead configuration, the base lead is brought out so that the device can be used as a conventional BJT with or without the additional light-sensitivity feature.*


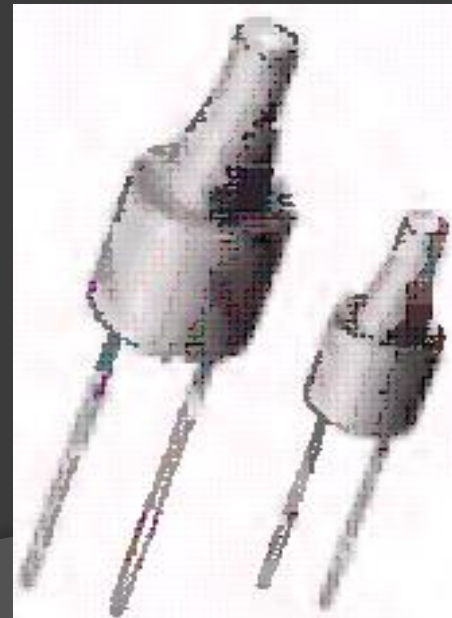
## 2. Two Lead Phototransistor:


*In the two-lead configuration, the base is not electrically available, and the device can be used only with light as the input. In many applications, the phototransistor is used in the two-lead version.*



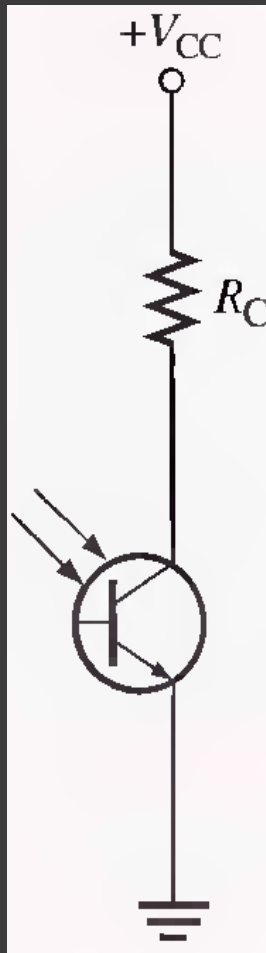


# Phototransistor Bias Circuit

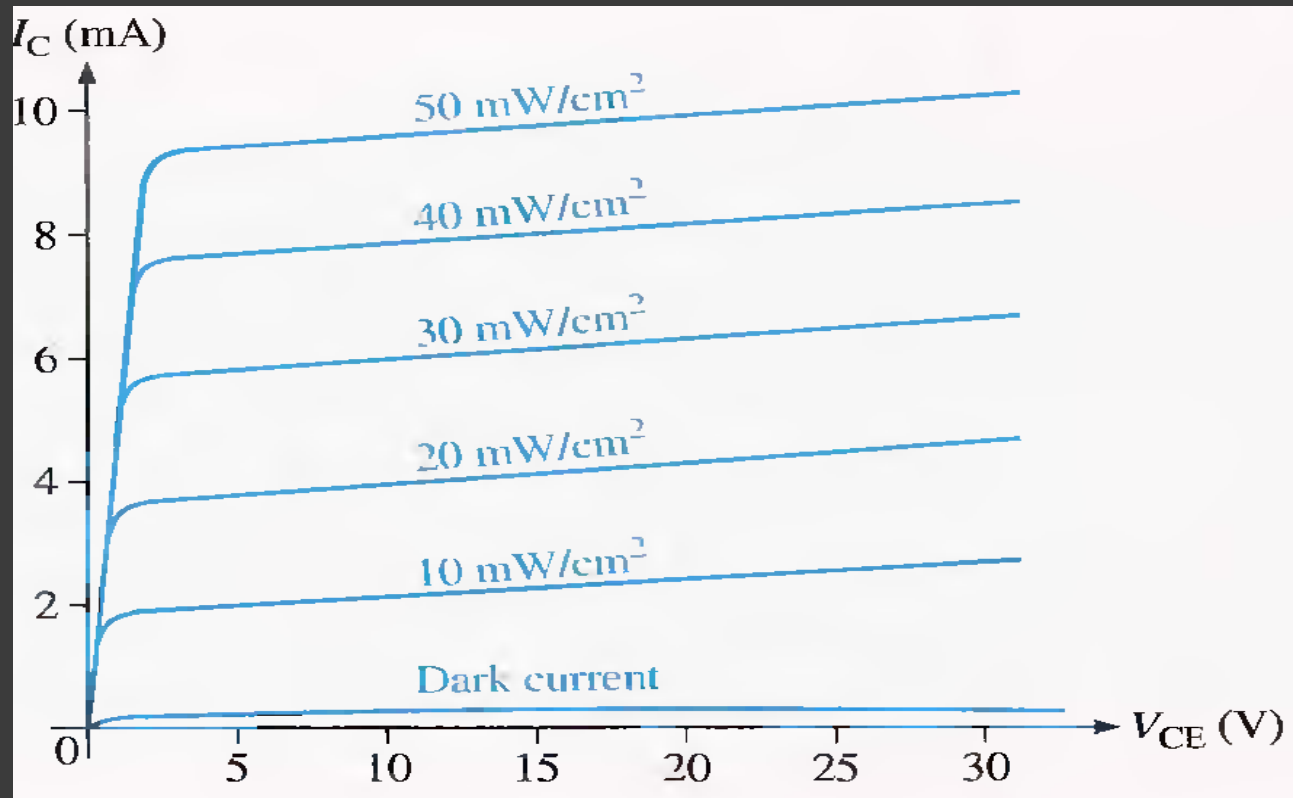**Typical collector characteristic curves. Notice that each individual curve on the graph corresponds to a certain value of light intensity (in this case, the units are  $mW/cm^2$ ) and that the collector current increases with light intensity.**



Percentage response

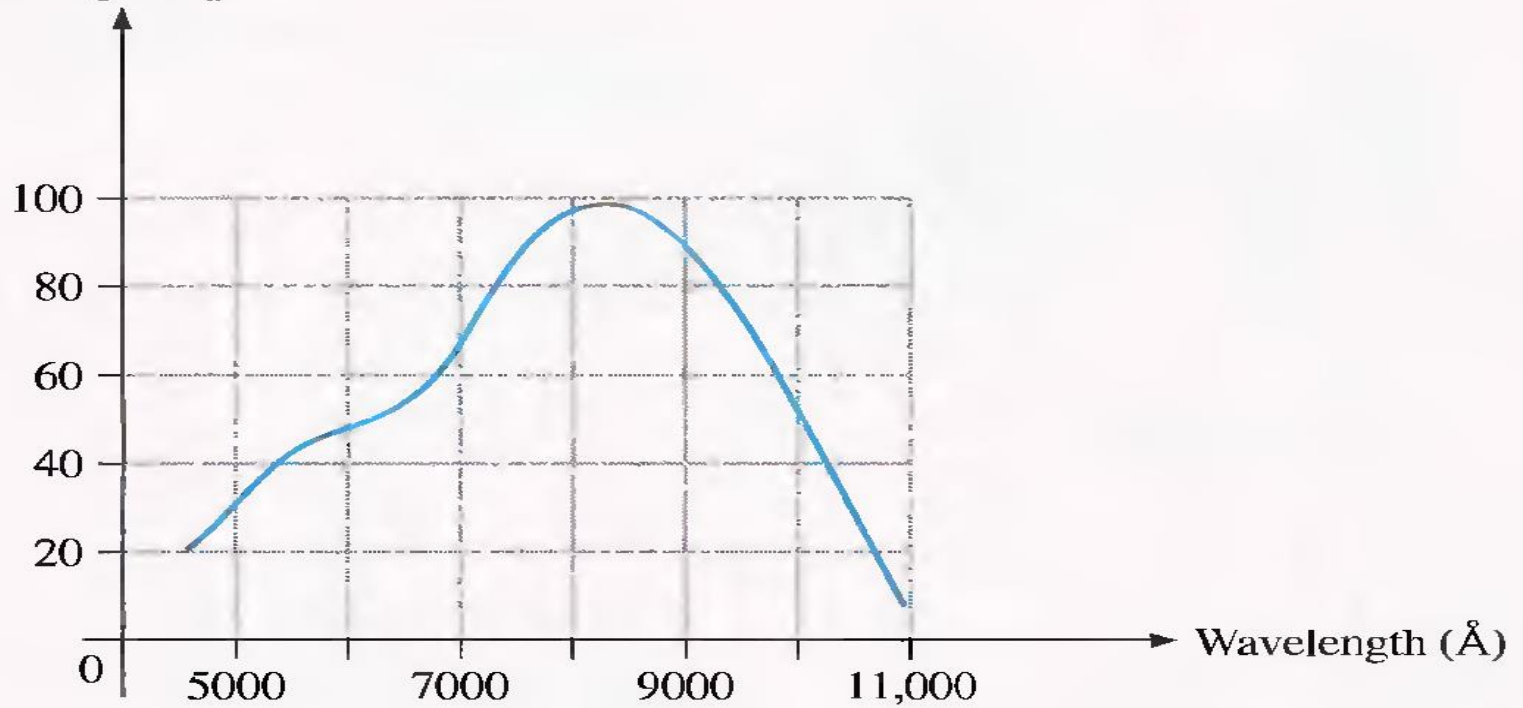

***Phototransistors are not sensitive to all light but only to light within a certain range of wavelengths. They are most sensitive to particular wavelengths, as shown by the peak of the spectral response curve in Figure.***